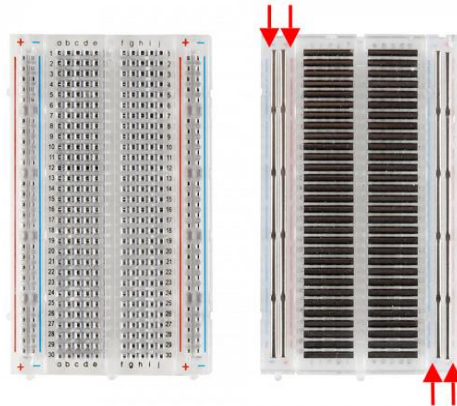


# 2 Lighting an LED

## What is a breadboard?


A breadboard is actually referring to a solderless breadboard. These are great units for making temporary circuits and prototyping, and they require absolutely no soldering.




Additional information <https://learn.sparkfun.com/tutorials/how-to-use-a-breadboard>
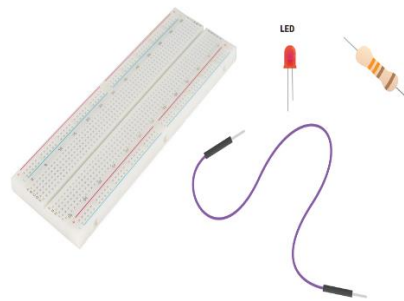
## Creating a circuit on a breadboard

**What you will need:** 1 Breadboard, 2 wires, 1 resistor and 1 LED



## Creating a Circuit on a Breadboard

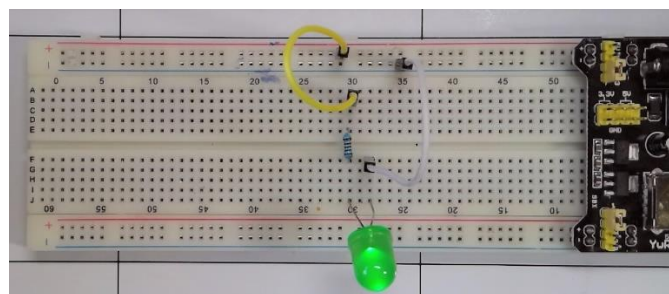

More on LEDs <https://learn.sparkfun.com/tutorials/light-emitting-diodes-leds>

